 


ECE3002 (VLSI SYSTEM DESIGN)

LAB TASK 4

Question:

Design a simple ALU for the following functions using Mux. Create the symbols and simulate the ALU, also find out the Propagation delay for each function.



S1	S0	Function
0	0	$A+B$
0	1	$\sim A$
1	0	$A \wedge B$
1	1	AB


Here we need to create a 4 x 1 multiplexer. This takes four inputs and based on the values of selection lines gives one output.

Consider the inputs to be I_0 , I_1 , I_2 and I_3 , the select lines be S_0 and S_1 , then the output will be:


$$Y = S_1'S_0'I_0 + S_1'S_0I_1 + S_1S_0'I_2 + S_1S_0I_3$$

We implement this in Cadence using four 3-input AND gates and 2 2-input OR gate in CMOS logic with sizing ratio of 3:1.


Now the **MUX** schematic will be:

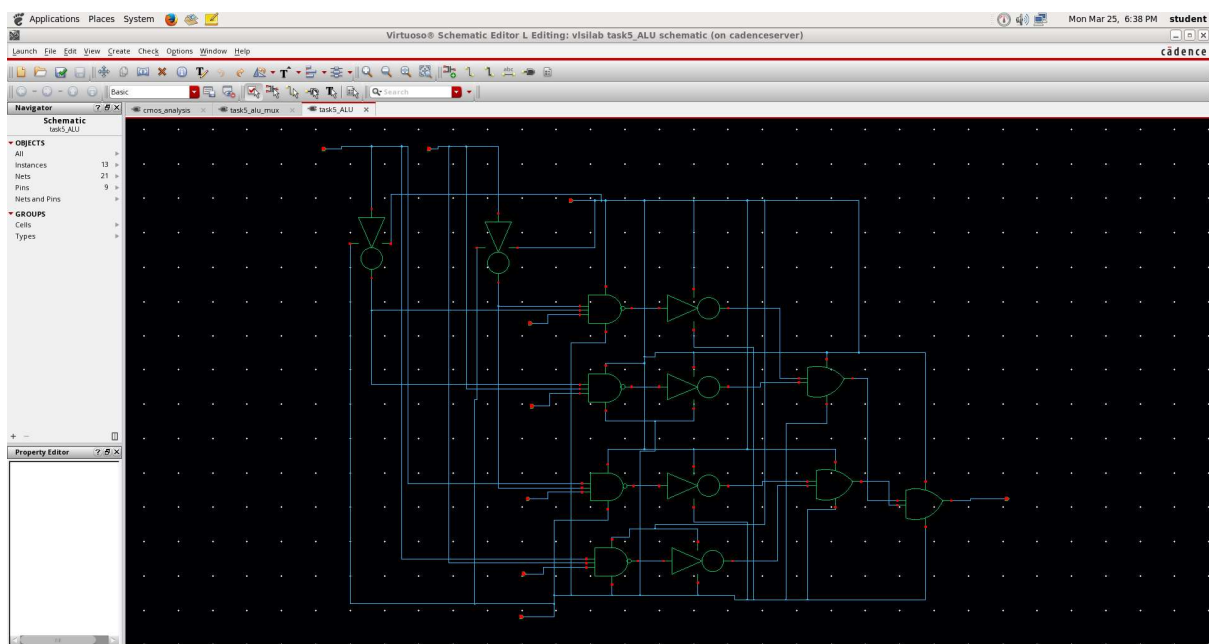

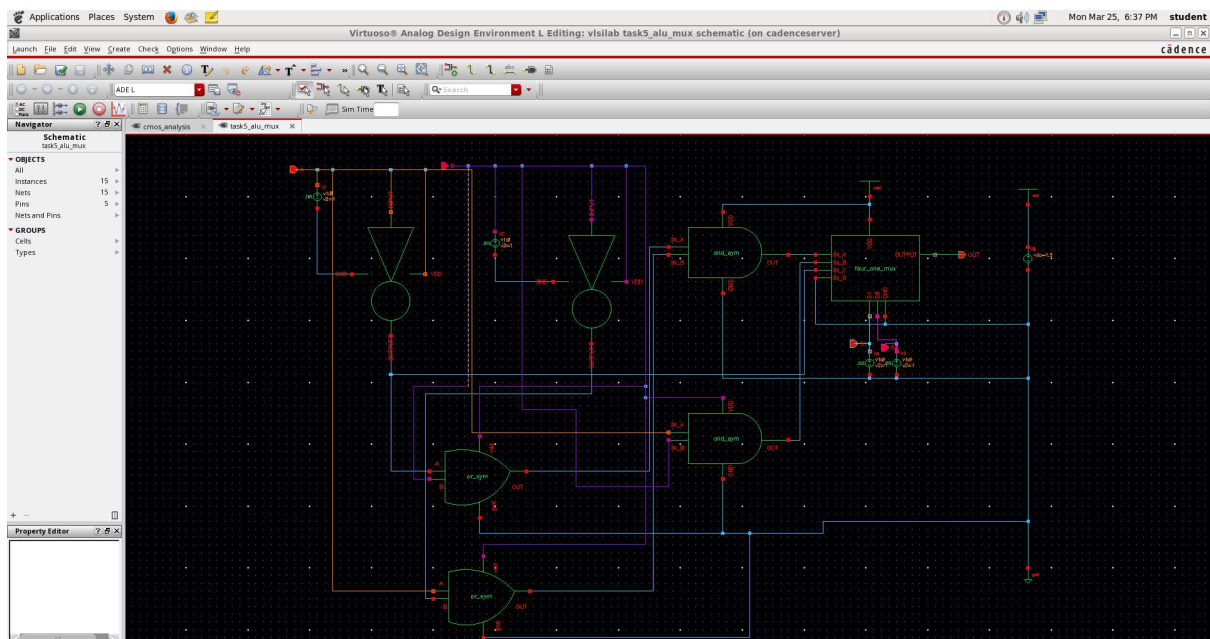Now the complete circuit to Implement the ALU is:



 On running this circuit, we observe the following output:



The output truth table is:

S1	S0	Function
0	0	A+B
0	1	$\sim A$
1	0	$A \wedge B$
1	1	AB

This is the required output.